

333356(33)

B. E. (Third Semester) Examination,  
Nov.-Dec. 2016

(New Scheme)

(IT Branch)

DIGITAL ELECTRONICS and LOGIC DESIGN

Time Allowed : Three hours

Maximum Marks : 80

Minimum Pass Marks : 28

Note : Attempt all questions. Part (a) from each question is compulsory. Attempt any two parts from (b), (c) and (d) of each question.

Unit-I

1. (a) Define K-map.

2

333356(33)

PTO

[ 2 ]

- (b) Simplify the Boolean expression by using K-map

$$F(W, X, Y, Z) = \sum m(2, 3, 8, 10, 11, 12, 14, 15)$$

with logic diagram also.

7

- (c) Simplify by the Tabular method.

7

$$F = \sum m(0, 1, 2, 5, 6, 7, 8, 9, 10, 14)$$

- (d) Write short notes on : (any two)

7

(i) Demorgan's Theorem

(ii) Self complementing code & ASCII code

(iii) Universal Gate

Unit-II

2. (a) What is Logic Family?

2

- (b) Explain Totem pole and open collector condition in TTL with circuit diagram.

7

- (c) Define different parameters of Logic Family.

7

- (d) Explain the working of CMOS inverter giving its circuit diagram & explain CMOS NOR gate function.

7

[ 3 ]

Unit-III

3. (a) Difference between Combinational Circuit & Sequential Circuit. 2
- (b) Explain serial adder with require diagram. 7
- (c) Explain full subtractor. 7
- (d) Define Multiplexer and solve the boolean expression using 8 : 1 MUX. 7
- $$F(A, B, C, D) = \sum m(0, 1, 2, 4, 5, 7, 9, 11, 13, 15)$$

Unit-IV

4. (a) Define Latches. 2
- (b) What is Shift Register? Give its types. 7
- (c) Design a T-type counter that goes through states 0, 3, 5, 6, 0..... Is the counter self-starting. 7
- (d) Design a BCD counter with JK flip flop. 7

Unit-V

333356(33)

PTO

[ 4 ]

5. (a) What are the different application of ROM? 2
- (b) Difference among PROM, PLA and PAL. 7
- (c) A combinational circuit is defined by the function
- $$F_1(A, B, C) = \sum(3, 5, 6, 7)$$
- $$F_2(A, B, C) = \sum(0, 2, 4, 7)$$
- Implement the circuit with the PLA having 3 inputs, 4 product terms & two outputs. 7
- (d) Difference between Meelay machine and Moore machine with example. 7