

Chapter 1

- | | | |
|---|--|---|
| 1 | Compare BCD with Binary. | 2 |
| 2 | What is a Hamming Code ? Assume that the data has been encoded in a 7 bit even parity hamming code and number 1011011 is received. Find out the bit in error. What will be the corrected code? | 7 |
| 3 | Simplify the expression using K-map.
$F = \sum m (0,2,4,5,6,7,8,10,11,12,14,15)$
Also realize the expression using AOI logic. | 7 |
| 4 | Simplify the following Boolean Expression using tabulation method.
$F(A,B,C,D) = \sum m (0,2,3,6,7,8,10,12,13)$
Draw Prime implicant chart and find essential prime implicants. | 7 |

Chapter 2

- | | | |
|---|---|---|
| 1 | Define fan-in and fan-out. | 2 |
| 2 | Discuss TTL logic family and also give detail of Totem pole output driver. | 7 |
| 3 | What is ECL logic? Why it is not popular? Give advantages and disadvantages of it. | 7 |
| 4 | Give the various characteristics of digital ICs based on which the performance of IC's can be compared? | 7 |

Chapter 3

- | | | |
|---|---|---|
| 1 | Mention the difference between Decoder and Demultiplexer. | 2 |
| 2 | Design a code converter that converts a decimal digit from 8421 code. | 7 |

- | | | |
|---|--|---|
| 3 | Design a 3 bit odd parity generator and checker. | 7 |
| 4 | Implement the following Boolean function using 8:1 multiplexer :
$F(A, B, C, D) = \sum m(0,1,3,4,8,9,15)$ | 7 |

Chapter 4 CSVТУonline.com

- | | | |
|---|--|---|
| 1 | Compare combinational and sequential circuits. | 2 |
| 2 | What are the advantages of JK flipflop over an SR flip flop ?
Construct the clocked JK flip flop using only NAND gates. | 7 |
| 3 | Design a mod-5 synchronous binary up-counter using T-flip flop. | 7 |
| 4 | Design and implement a mod-10 asynchronous counter using T-flipflop. | 7 |

Chapter 5 CSVТУonline.com

- | | | |
|---|--|---|
| 1 | Give difference between RAM and ROM. | 2 |
| 2 | Explain briefly different types of ROM's. | 7 |
| 3 | Draw and explain block diagram of PLA. | 7 |
| 4 | (i) What is major difference between Mealy and Moore Machine?
(ii) What are applications of finite state machine model? | 7 |